



**Department of Electrical and Computer Engineering
Utah State University**

**ECE 5930/6930: VLSI Testing and Verification
Created By: Shayan (Sean) Taheri**


**Homework 03
Solution Outline**

Answer 1.

We level order the signals and proceed as follows:


Step no.	Action	Signals											D front.	Impl. stack
		A	B	C	d	e	f	g	Y	h	k	Z		
1	Fault Activation							0 0	\overline{D}				k	$g = 0$
	Immediate impl.				0 0			0 0	\overline{D}				k	$g = 0$
	Immediate impl.	1	1	0 0				0 0	\overline{D}				k	$g = 0$
	Immediate impl.	1	1	0 0	0 0			0 0	\overline{D}				k	$g = 0$
	Immediate impl.	1	1	0 0	0 0	0 0		0 0	\overline{D} 0				ϕ	$g = 0$
	Immediate impl.	1	1	0 0	0 0	0 0	0 0	0 0	\overline{D} 0 1				ϕ	$g = 0$

The fault is redundant because the D-frontier disappeared and there is no backtracks. Signals are shown in the following figure:

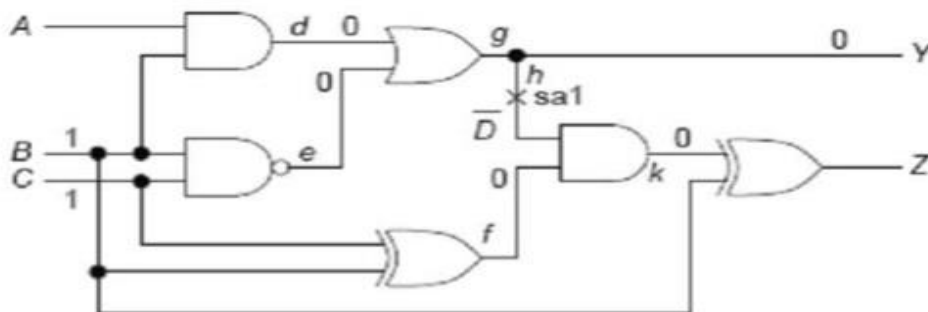

Answer 2.

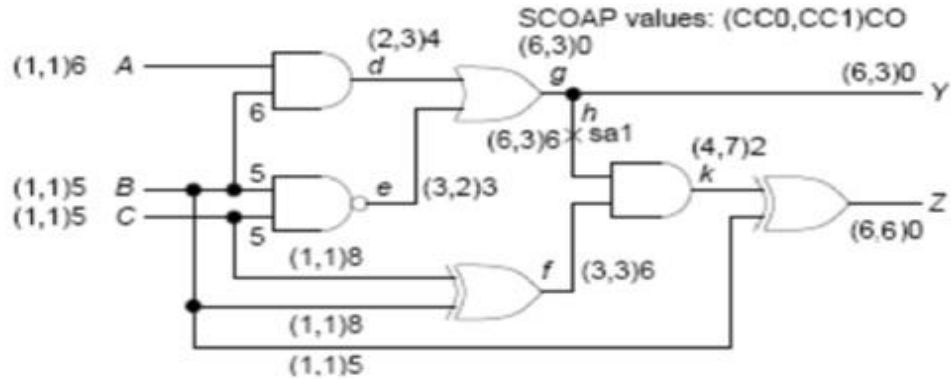The figure below shows the SCOAP testability measures used for guiding PODEM.



The steps of the PODEM algorithms are recorded in the following table:


Step No.	Objective	Action	Imp. stack	Implied signal values A B C d e f g h k Y Z	D front.	X path
1	$g = 0$	Backtrace	$B = 1$	1	ϕ	ok
2	$g = 0$	Backtrace	$C = 1$ $B = 1$	1 1 0 0 0 0 1	ϕ	none
3	$g = 0$	Backtrack	$C = 0$ $B = 1$	1 0 1 1 1 1 1 0	ϕ	none
4	$g = 0$	Backtrack	$B = 0$	0 0 1 1 1 1	ϕ	none
5	$g = 0$	Backtrack	Empty			
Algorithm termination: Objective $g=0$ is impossible; fault h s-a-1 is redundant.						

Explanation: an X-path is a path from the fault site to a PO, such that the signals on it are either faulty states or undetermined. An "OK" for X-path in the table means that one or more such paths exist. Having no X-path is a reason for backtracks because its existence is a necessary condition for the detection of the fault. When a series of backtracks leads to an empty stack, it indicates that the objective $g = 0$ is impossible. As a result, **the fault h (stuck-at-1) cannot be activated and, hence, it is redundant.** Meanwhile, there is three backtracks.

Answer 3.

Step	Action	Impl. stack	Forward implications	D-frontier
1	Fault act.	$h = 0$	$h = 0, h1 = \overline{D}, i2 = 0$	$i1$
2	D-prop.	$g1 = 1, h = 0$	$g1 = 1, h = 0, h1 = \overline{D}$ $i1 = \overline{D}, i2 = 0$	PO
3	Justify	$e1 = 1, g1 = 1$ $h = 0$	$e1 = 1, g1 = 1, h = 0$ $h1 = \overline{D}, i1 = \overline{D}, i2 = 0$	PO
4	Justify	$a = 1, b = 1$ $e1 = 1, g1 = 1$ $h = 0$	$a = 1, b = 1, e1 = 1, g1 = 1$ $e2 = 1, g1 = 1, g2 = 1$ $h = 0, h1 = \overline{D}, i1 = \overline{D}$ $i2 = 0$	PO
Test found: $(a, b, c, d, h, k) = (1, 1, X, X, 0, X); i1 = \overline{D}$				

The following figure shows the circuit and the signal values specified by D-algorithm.

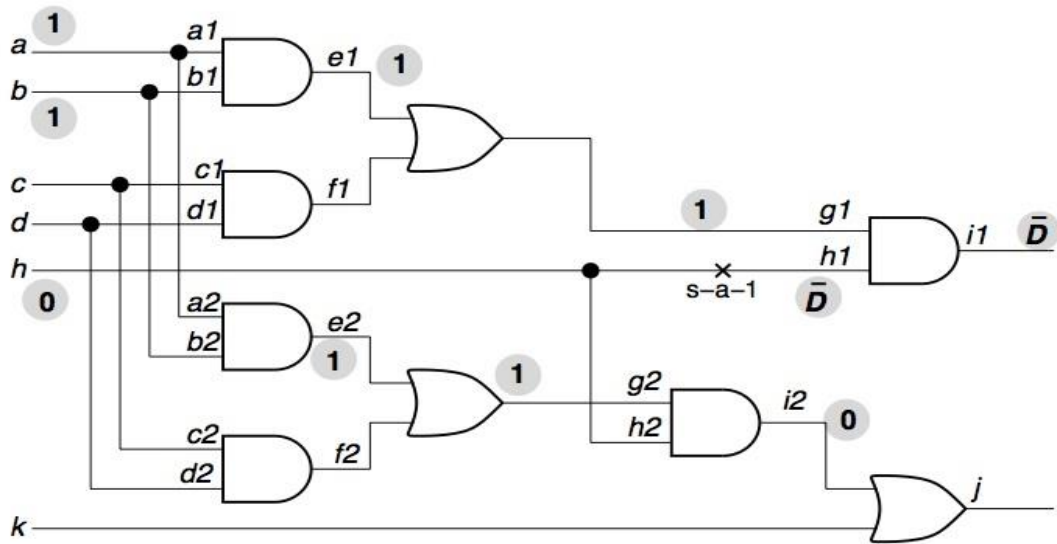

Answer 4.

The following table gives the steps of PODEM algorithm:

Step No.	Objective	Action	Imp. stack	Implied signal values <i>ABCDEFghklmpqsruwZ</i>	<i>D</i> front.	<i>X</i> path
1	$g = 0(\bar{D})$	Backtrace	$C = 0$	$C = 0, h = 0$	ϕ	ok
2	$g = 0(\bar{D})$	Backtrace	$D = 0$ $C = 0$	$C = 0, D = 0, g = 0(\bar{D})$ $h = 0, k = 0, m = 0, u = 0$	ϕ	none
3	$g = 0(\bar{D})$	Backtrack	$D = 1$ $C = 0$	$C = 0, D = 1, g = 1, h = 0$ $k = 1, m = 1, p = 0, q = 1, r = 0$	ϕ	none
4	$g = 0(\bar{D})$	Backtrack	$C = 1$	$C = 1, g = 1, h = 1, m = 1$ $p = 0, q = 1, r = 0$	ϕ	none
5	$g = 0(\bar{D})$	Backtrack	Empty			
Algorithm termination: $g = 0(\bar{D})$ with <i>X</i> -path impossible; fault g s-a-1 is redundant. 3 backtracks.						