

## Department of Electrical and Computer Engineering Utah State University

# ECE 5930/6930: VLSI Testing and Verification Instructor: Dr. Roy

Homework 04
Solution Outline

### Answer 1.

The SCOAP values are shown in the Figure 1:

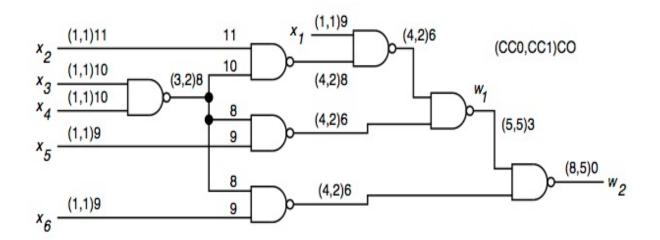


Figure 1: Combinational SCOAP Measures

### Answer 2.

The SCOAP values are shown in the Figure 2:

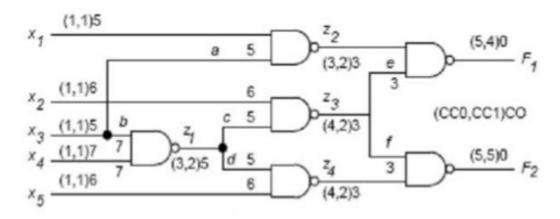


Figure 2: Combinational SCOAP Measures

### Answer 3.

The steps of calculation for SCOAP testability measures are shown in the three figures that follow. Combinational measures are shown as (CCO, CC1) CO and sequential measures as (SCO, SC1) SO.

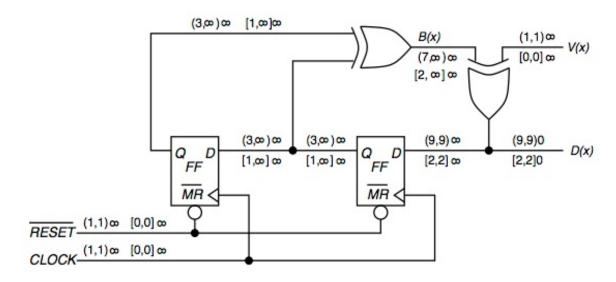


Figure 3: Initialization and First Controllability Pass

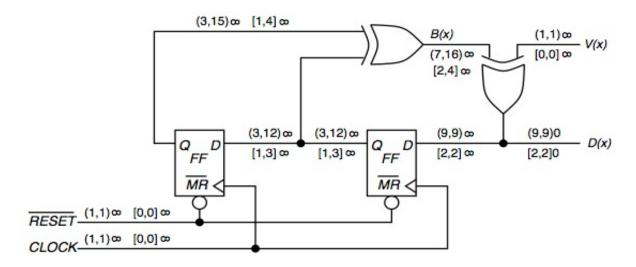


Figure 4: Converged Controllability Values

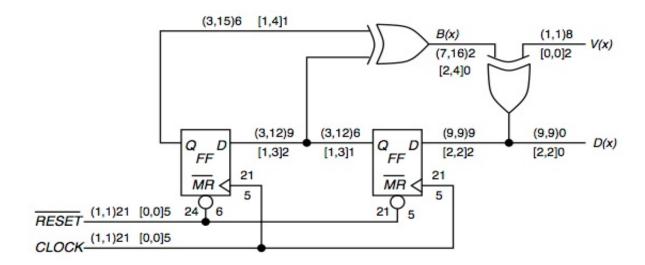


Figure 5: All Controllability and Observability Values